

## CS2100 Assignment 3 Answer Book

Name:	<i>Lily Jia Wei</i>
Student ID:	<i>A0255479M</i>
Tutorial Group Number:	<i>13</i>

Save this file as AxxxxxxxY.pdf and submit on Canvas. You do NOT need to create a zip file.

You will forfeit up to 3 marks if you do not fill your particulars above, or do not follow the submission instructions.

Submission information: \_\_\_\_\_ / 3

### Question 1. (6 MARKS)

- (a) (2 marks)  $F(A,B,C,D) = \Sigma m( \textcolor{blue}{6, 15} )$
- (b) (2 marks)  $G(A,B,C,D) = \Sigma m( \textcolor{blue}{8, 10, 12} )$
- (c) (2 marks)  $H(D,C,B,A) = \Sigma m( \textcolor{blue}{10, 11, 15} )$

Q1 Total: \_\_\_\_\_ / 6

### Question 2. (6 MARKS)

- (a) (2 marks)  $X(A,B,C) = \Pi M( \textcolor{blue}{0, 3, 6, 7} )$
- (b) (2 marks)  $Y(A,B,C,D) = \Pi M( \textcolor{blue}{0, 1, 2, 3, 6, 7, 8, 10, 11, 13, 14, 15} )$
- (c) (2 marks)  $Z(C,B,A) = \Pi M( \textcolor{blue}{1, 2, 4, 6} )$

Q2 Total: \_\_\_\_\_ / 6

### Question 3. (7 MARKS)

- (a) (3 marks)

$$F = \textcolor{blue}{A' + B' \cdot C'}$$


$$G = \textcolor{blue}{A' \cdot B + B \cdot C' + A \cdot B' \cdot C}$$

$$H = \textcolor{blue}{C}$$

- (b) (2 marks)

"The circuit converts a 3-bit *Sign and Magnitude* to 3-bit *excess 4 code*."

- (c) (2 marks)

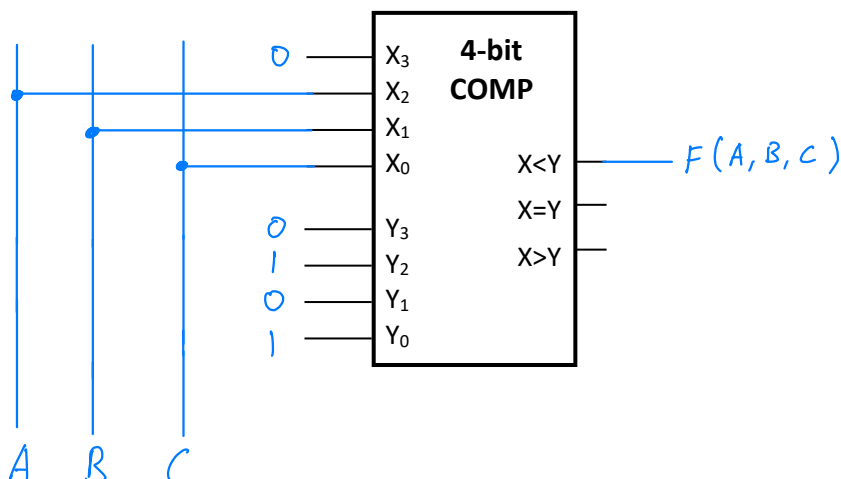


Q3 Total: \_\_\_\_\_ / 7


**Question 4. (7 MARKS)**

(a) (2 marks)  $F(A,B,C,D) = B \cdot C' \cdot D' + A \cdot C' + A \cdot B \cdot D'$

(b) (2 marks)

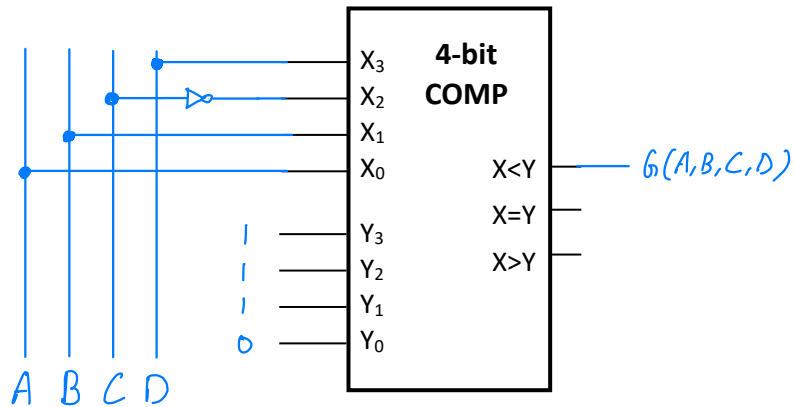

(c) (3 marks)

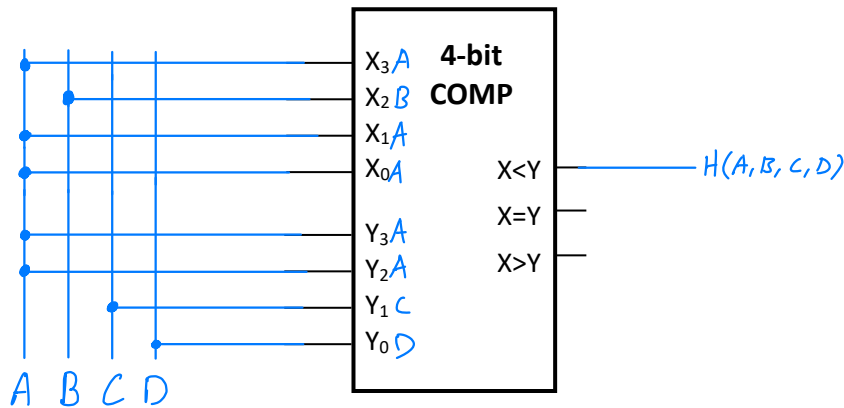

Q4 Total: \_\_\_\_\_ / 7

**Question 5. (5 MARKS)**

$$F_2 = A_7 + A_6 + A_5 + A_4$$

$$F_1 = A_7 + A_6 + (A'_5 \cdot A'_4 \cdot A_3) + (A'_5 \cdot A'_4 \cdot A_2)$$

$$F_0 = A_7 + (A'_6 \cdot A_5) + (A'_6 \cdot A'_4 \cdot A_3) + (A'_6 \cdot A'_4 \cdot A'_2 \cdot A_1)$$

Q5 Total: \_\_\_\_\_ / 5

**Question 6. (6 MARKS)**

(a) (2 marks) State  $(111)_2$

(b) (2 marks) State  $(010)_2$

(c) (2 marks)  $(010)_2, (000)_2$

Q6 Total: \_\_\_\_\_ / 6

**Total Marks: \_\_\_\_\_ / 40** (To be filled by TA only)

=== END OF PAPER ===