

CS2100 Assignment 3 Answer Book

Name:	
Student ID:	
Tutorial Group Number:	

Save this file as AxxxxxxxY.pdf and submit on Canvas. You do NOT need to create a zip file.

You will forfeit up to 3 marks if you do not fill your particulars above, or do not follow the submission instructions.

Submission information: _____ / 3

Question 1. (6 MARKS)

- (a) (2 marks) $F(A,B,C,D) = \sum m(\quad \quad \quad)$
- (b) (2 marks) $G(A,B,C,D) = \sum m(\quad \quad \quad)$
- (c) (2 marks) $H(D,C,B,A) = \sum m(\quad \quad \quad)$

Q1 Total: _____ / 6

Question 2. (6 MARKS)

- (a) (2 marks) $X(A,B,C) = \prod M(\quad \quad \quad)$
- (b) (2 marks) $Y(A,B,C,D) = \prod M(\quad \quad \quad)$
- (c) (2 marks) $Z(C,B,A) = \prod M(\quad \quad \quad)$

Q2 Total: _____ / 6

Question 3. (7 MARKS)

- (a) (3 marks)

$F =$


$G =$

$H =$

- (b) (2 marks)

“The circuit converts a 3-bit _____ to 3-bit _____.”

- (c) (2 marks)

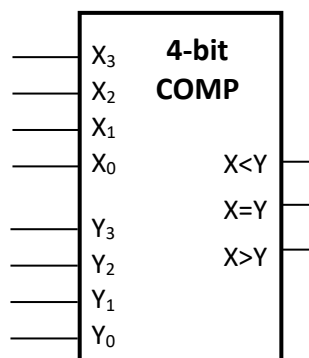


Q3 Total: _____ / 7


Question 4. (7 MARKS)

(a) (2 marks) $F(A,B,C,D) =$

(b) (2 marks)

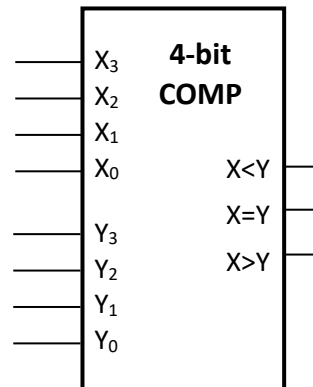

(c) (3 marks)

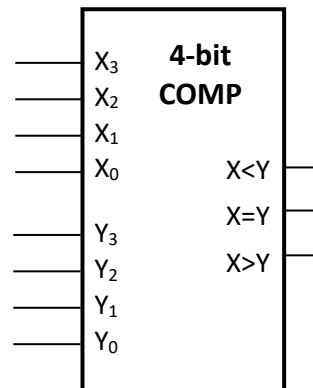

Q4 Total: _____ / 7

Question 5. (5 MARKS)

$$F_2 =$$

$$F_1 =$$

$$F_0 =$$

Q5 Total: _____ / 5

Question 6. (6 MARKS)

(a) (2 marks) State

(b) (2 marks) State

(c) (2 marks)

Q6 Total: _____ / 6

Total Marks: _____ / 40 (To be filled by TA only)

=== END OF PAPER ===